

# **CSE 2600**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Michael Hall

# Review Reading (from Mem. to Reg): Load

- Mnemonic: load word (lw)
- Format: lw t1, 8(s0)  
lw destination, offset(base)
- Address calculation: RAM index = add base address (s0) to the offset (8) = (s0 + 8)
- Result: t1 holds the data value at address (s0 + 8)  
I.e. t1 = RAM[s0+8]
- In terms of “register” array:  
REG[t1] = RAM[REG[s0]+8]  
REG[6] = RAM[REG[8]+8]
- Units: Memory is usually “byte addressable” and words are 4 bytes.  
So data is actually retrieved from RAM[REG[s0]+8] to RAM[REG[s0]+11]

# Reading (from Reg to Mem.): Store

- Mnemonic: store word (sw)
- Format: sw t1, 8(s0)  
sw source, offset(base)
- Address calculation: RAM index = add base address (s0) to the offset (8) = (s0 + 8)
- Result: t1 holds the data value at address (s0 + 8)  
I.e.  $\text{RAM}[\text{s0}+8] = \text{t1}$
- In terms of “register” array:  
 $\text{RAM}[\text{REG}[\text{s0}]+8] = \text{REG}[\text{t1}]$   
 $\text{RAM}[\text{REG}[\text{8}]+8] = \text{REG}[\text{6}]$
- **NOTE: Stores are the one case where the “thing on the left” is not the destination!**

# **Studio 6B: More Assembly (Functions & Memory)**

# **Chapter 6 & 7**

# ***Architectures: RISC-V***

- “Architecture”: Programmer’s view of CPU
- Fundamental data size: 32-bit “word”. CPU/ALU designed for 32-bit operations (Multiple 32-bit operations can be done to do larger operations)
- Memories
  - RAM: Big array of numbers; Uses 32-bit addresses
  - Registers: Array with 32, 32-bit values. Special names correspond to intended uses (Ex: a-registers, like a0, are for “arguments” to functions)
  - Instructions: Also 32-bit values; May be stored in RAM or separate memory



# Architectures: RISC-V

- Machine codes
  - “Substitution code”: Numbers represent concepts
  - RISC-V “Instruction Set Architecture” (ISA):
    - Formats are about data locations  
 (“addressing” / location of information needed)

# Architecture & MicroArchitecture

- Architecture: Blueprint of behavior based on assembly language
- Microarchitecture: Specific implementation(s)
  - Lots of variations possible with cost/performance tradeoffs
  - Ex: “Single Cycle” version vs. “Pipelined”
    - Single-Cycle: Each instruction is 1 (long) cycle
    - Multi-Cycle: Instructions take more than one cycle, but cycles are shorter and overall performance is better.


# Homework 5A: Part 1

 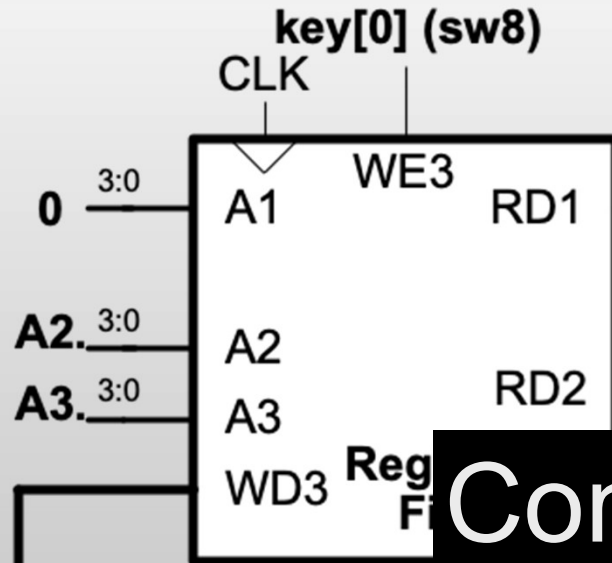


Control: You

Data path: Hardware

# Simple (Single-Cycle) RISC-V Computer

 
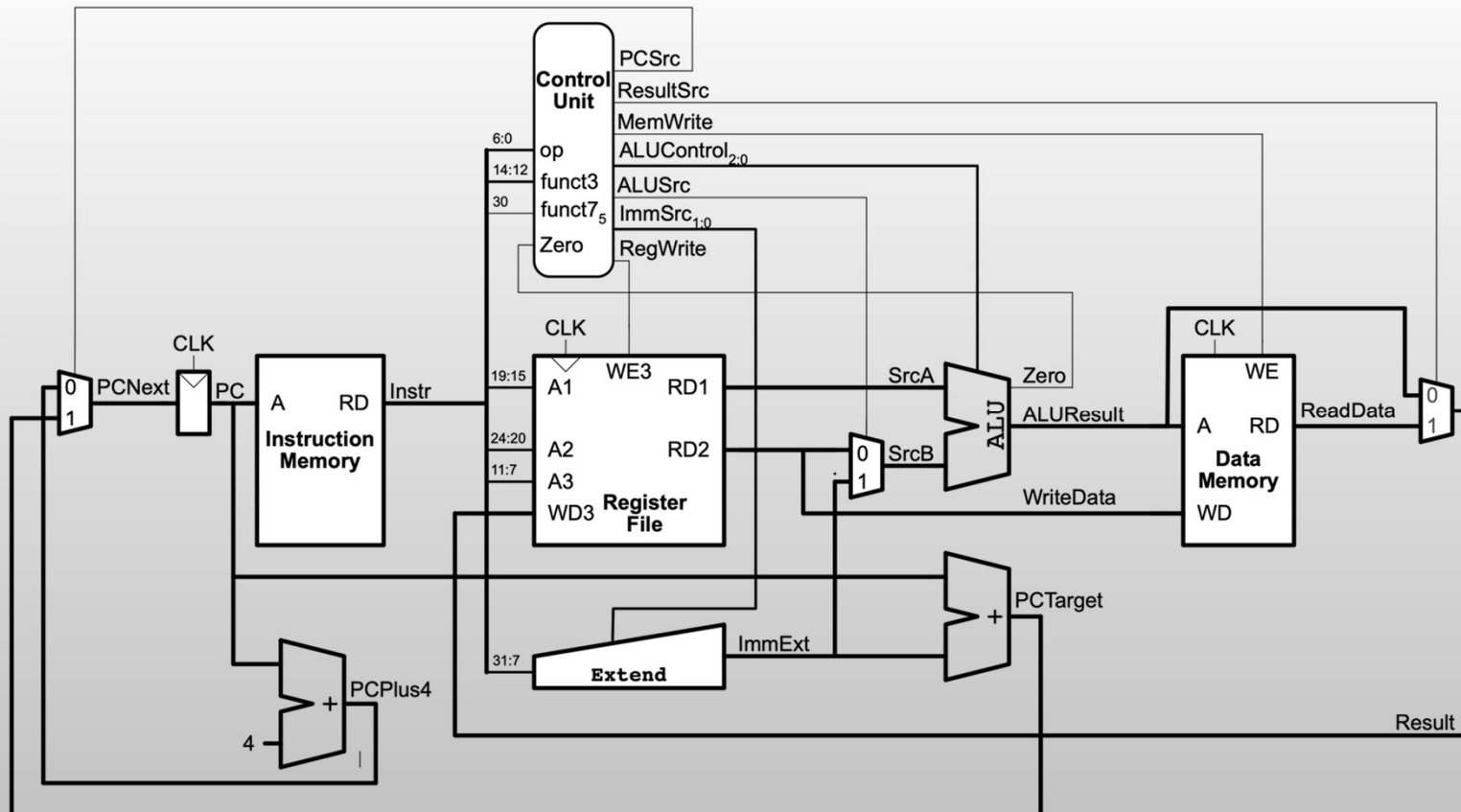
# Simple (Single-Cycle) Control vs. Datapath



# The Problem

**Find  $x$  such that  $2^x = 128$**

pow in s0; x in s1

**Problem: Find x such that  $2^x = 128$**

```
// determines the power  
// of x such that 2x = 128  
int pow = 1;  
int x = 0;
```


```
while (pow != 128) {
```

```
    pow = pow * 2;
```


```
    x = x + 1;
```

```
}
```


# Behavior: Parts of CPU Model

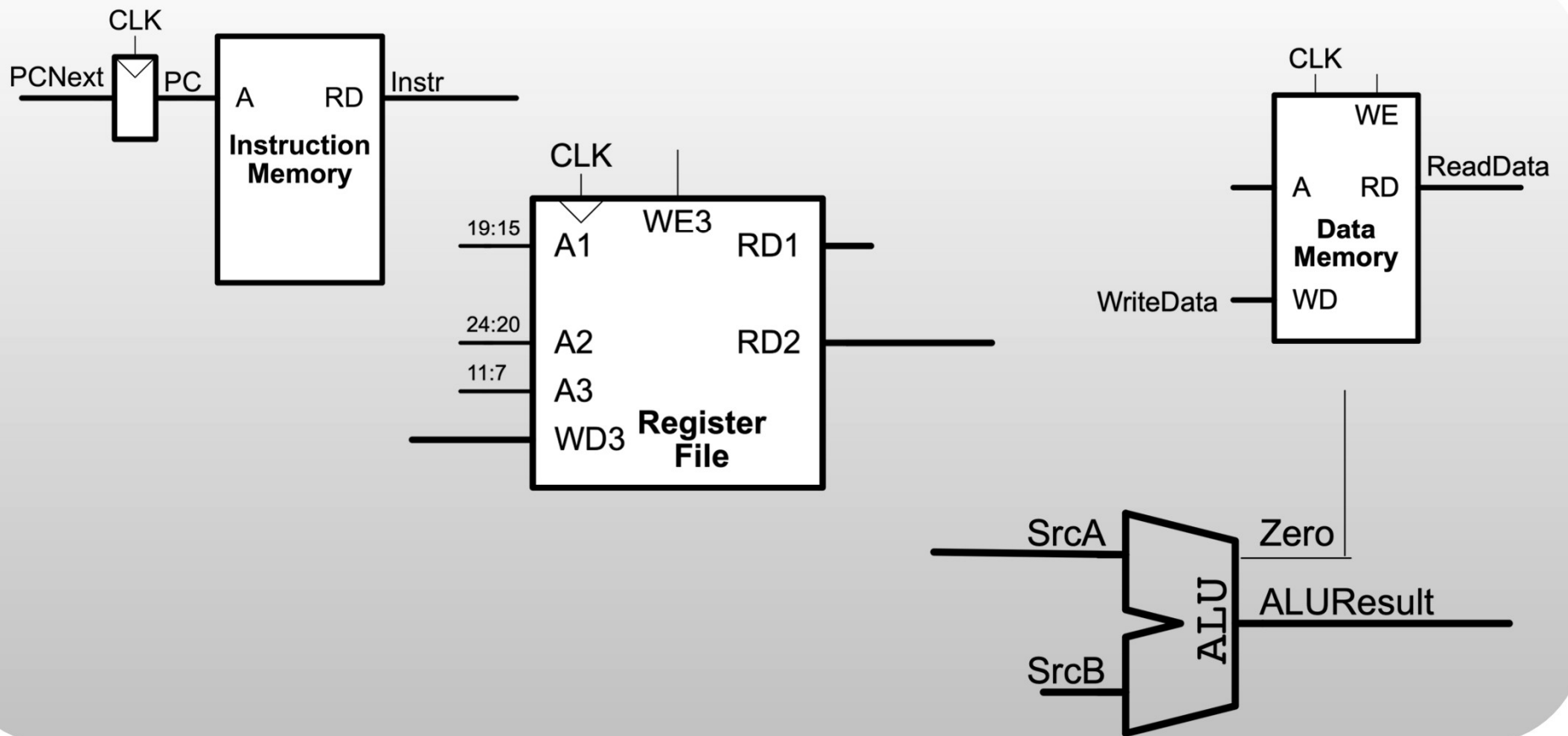


# Behavior: Parts of CPU Model

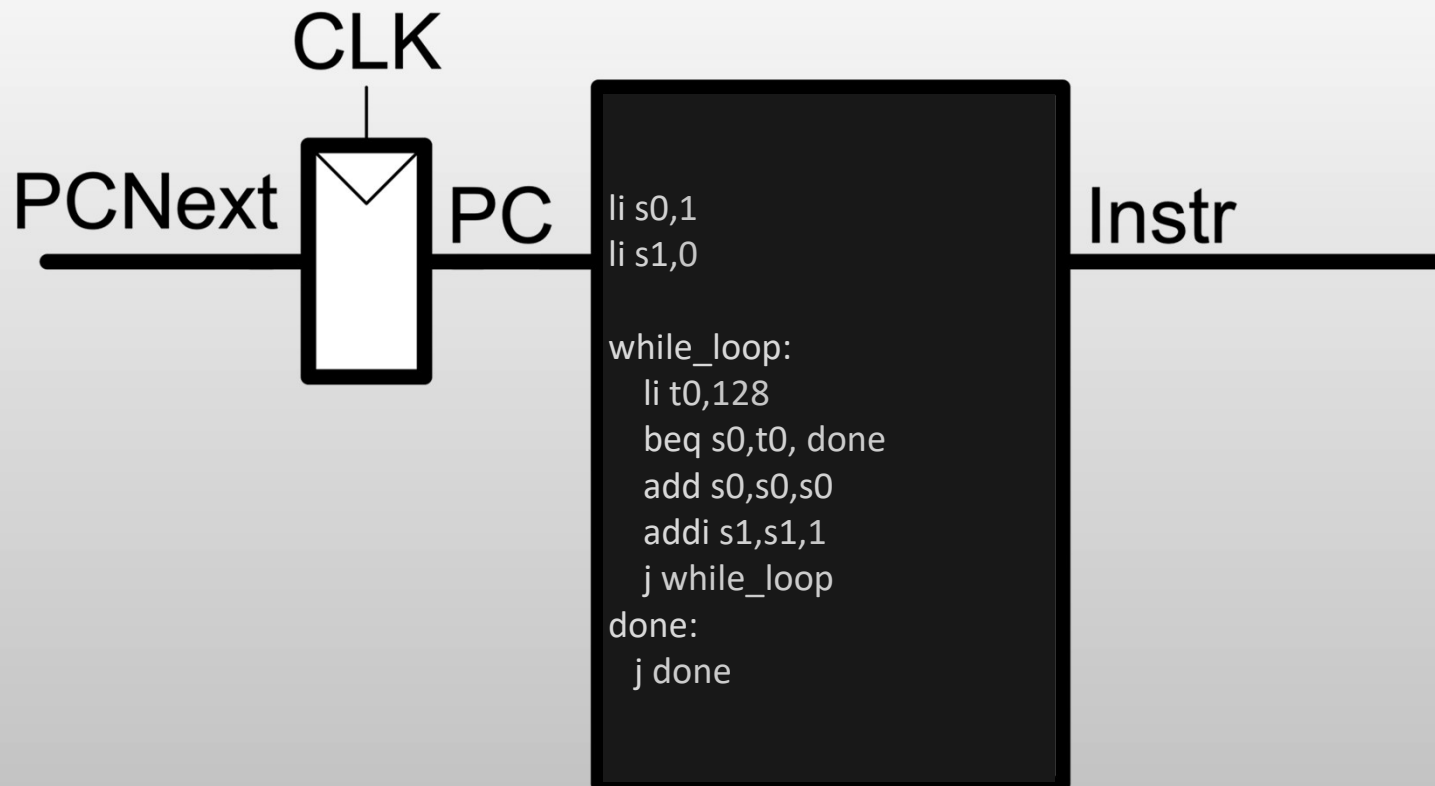


# Behavior: Parts of CPU Model

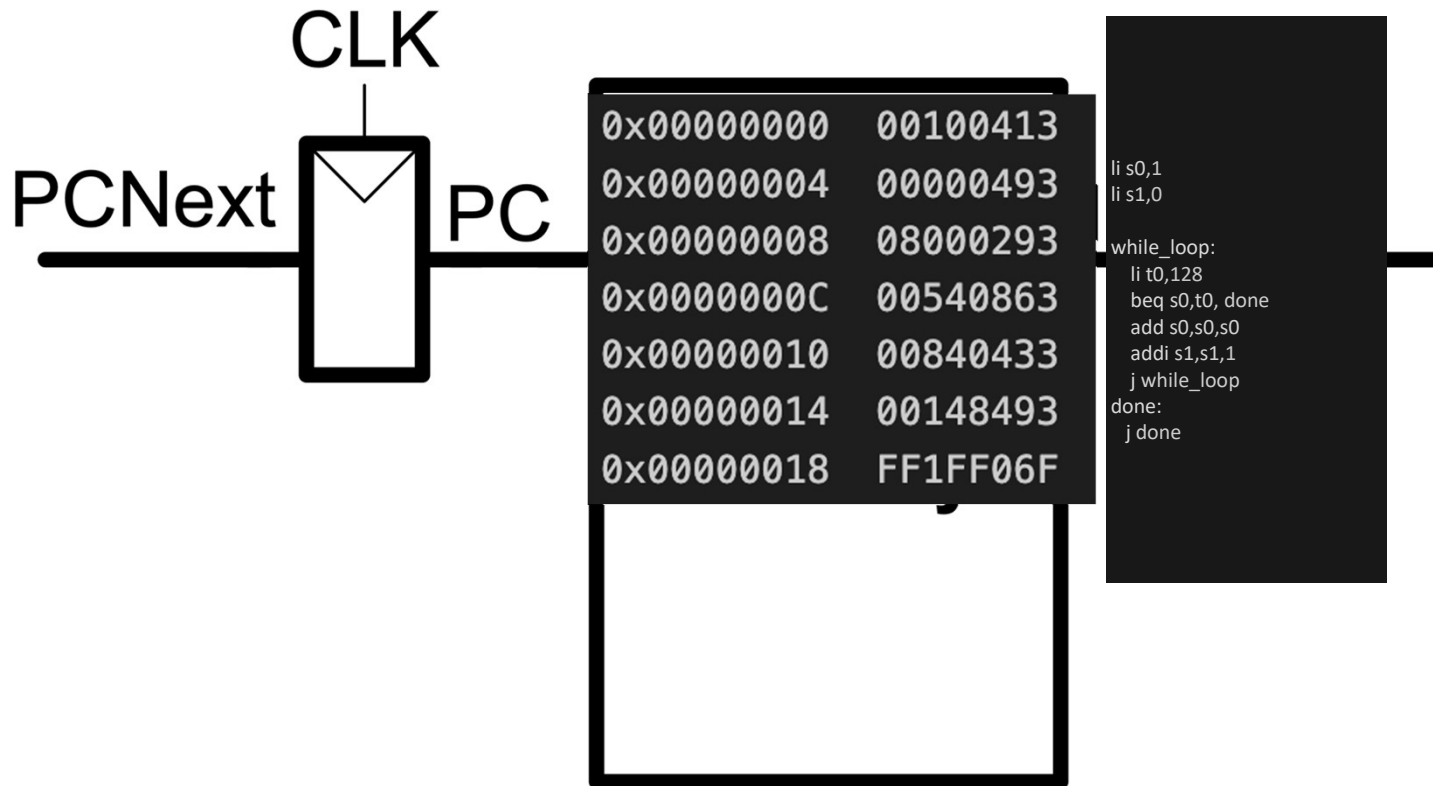


# Behavior: Parts of CPU Model

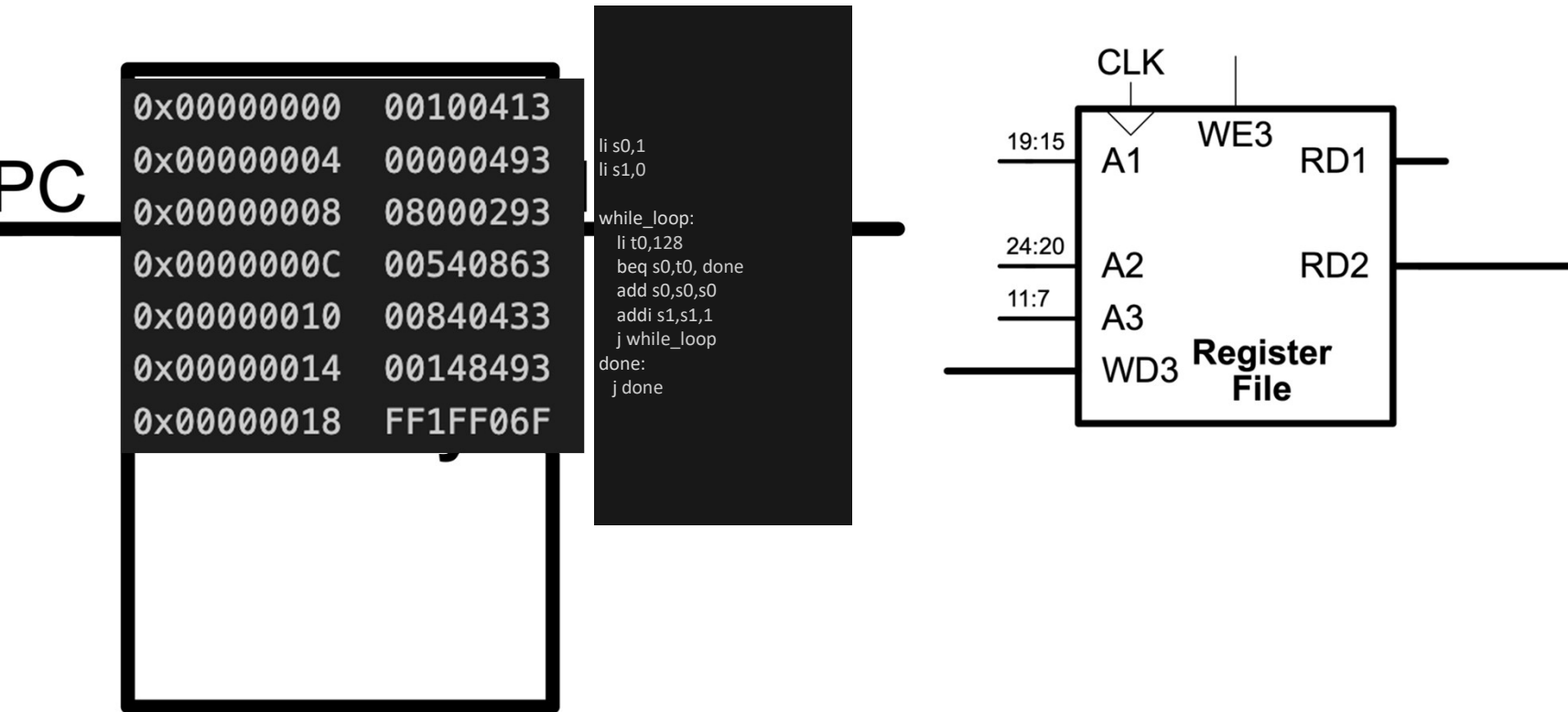

# Behavior: Parts of CPU Model

 

# Behavior: Parts of CPU Model

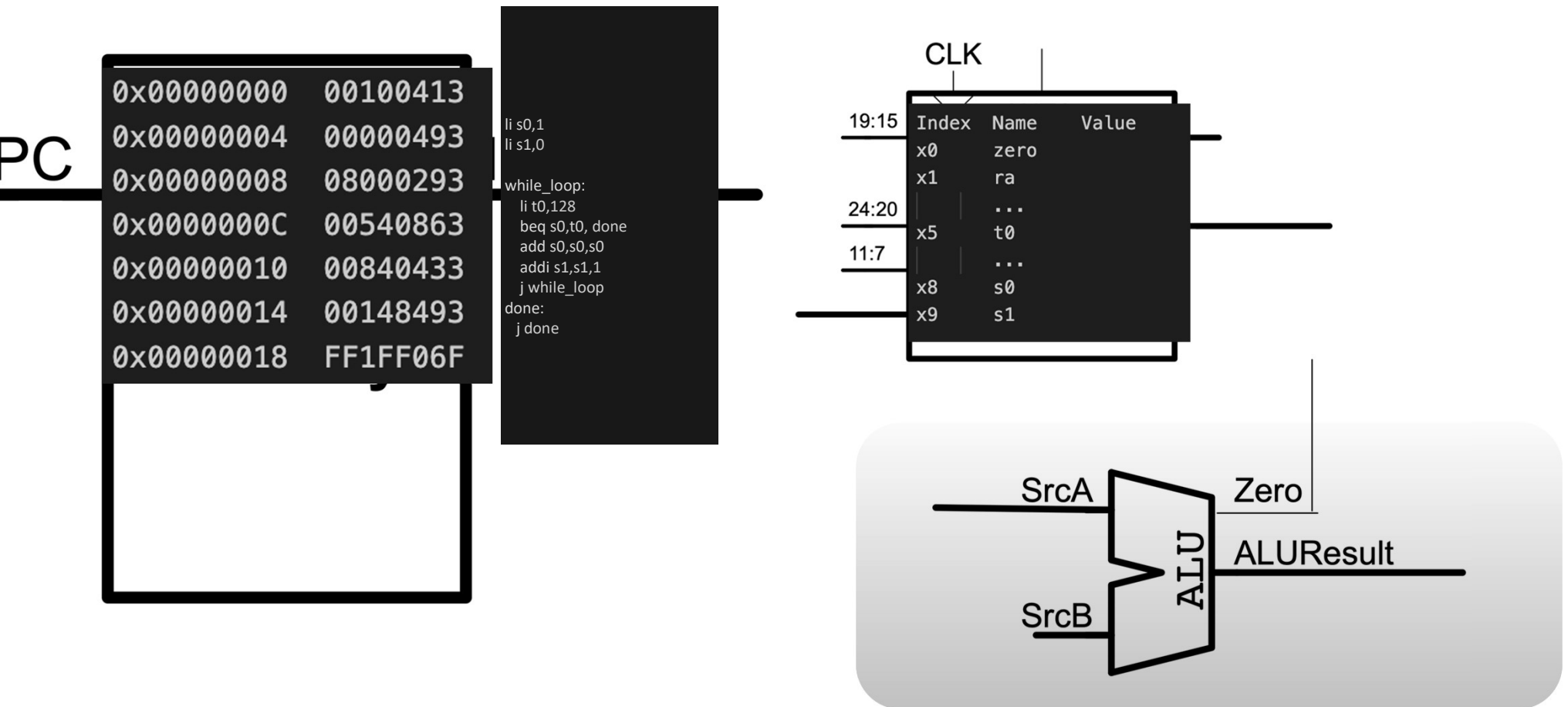

```

0x00000000  00100413
0x00000004  00000493
0x00000008  08000293
0x0000000C  00540863
0x00000010  00840433
0x00000014  00148493
0x00000018  FF1FF06F

```


```

li s0,1
li s1,0
while_loop: li t0,128
             beq s0,t0, done
             add s0,s0,s0
             addi s1,s1,1
             j while_loop
done: i done

```


# Model

| Index | Name | Value |
|-------|------|-------|
| x0    | zero |       |
| x1    | ra   |       |
|       | ...  |       |
| x5    | t0   |       |
|       | ...  |       |
| x8    | s0   |       |
| x9    | s1   |       |

 

 
# Simple, Single-Cycle RISC-V Computer

Identify items that are part of the “propagation delay” of an instruction.  
(Estimate upper bound that needs to be used to determine clock cycle)



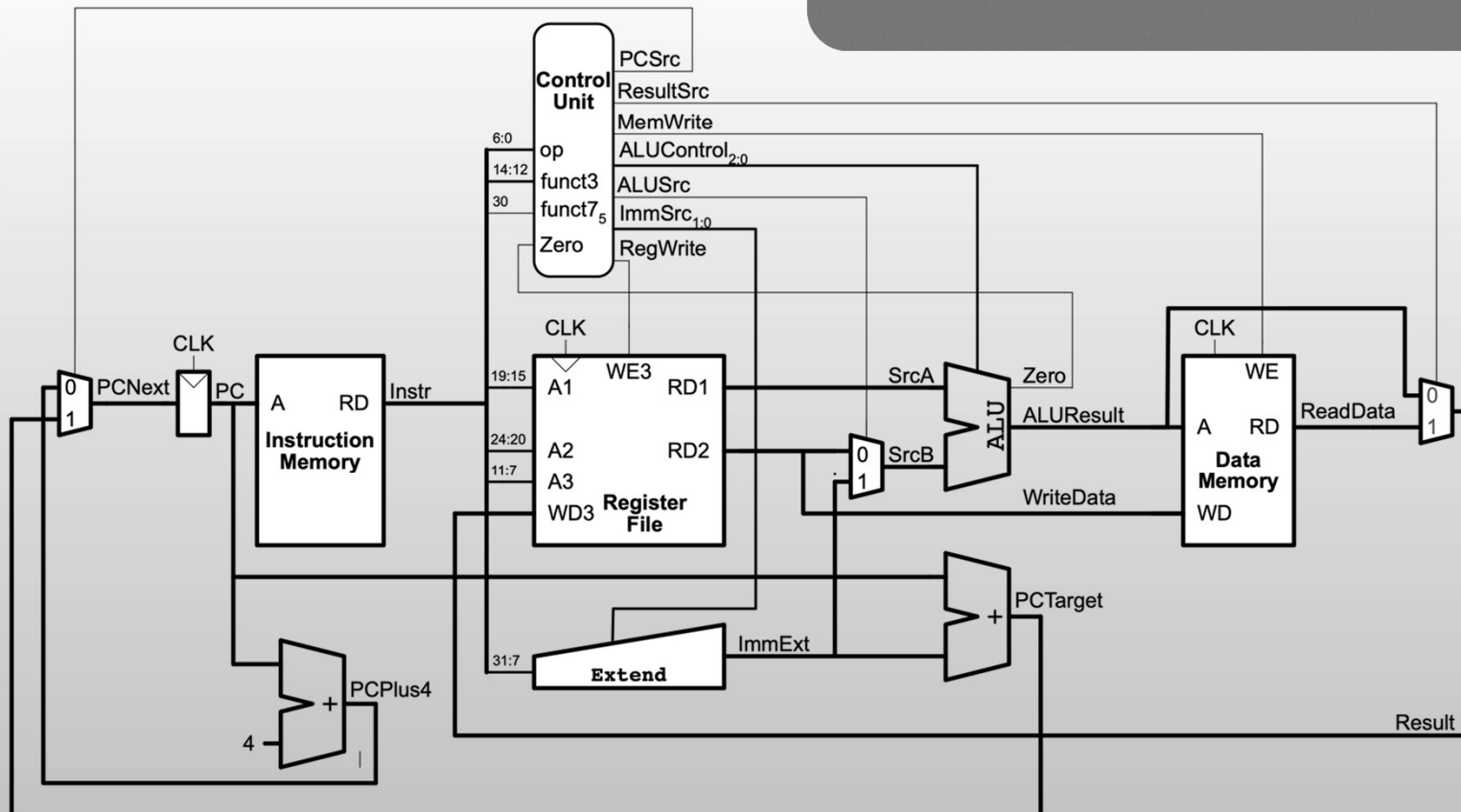
# Simple, Single-Cycle

Describe behavior of all elements and any required control signals for add t0,t1,t1



 
# Simple, Single-Cycle

Describe behavior of all elements and any required control signals for  
beq t0,zero,loop  
(Assume t0 is 0)



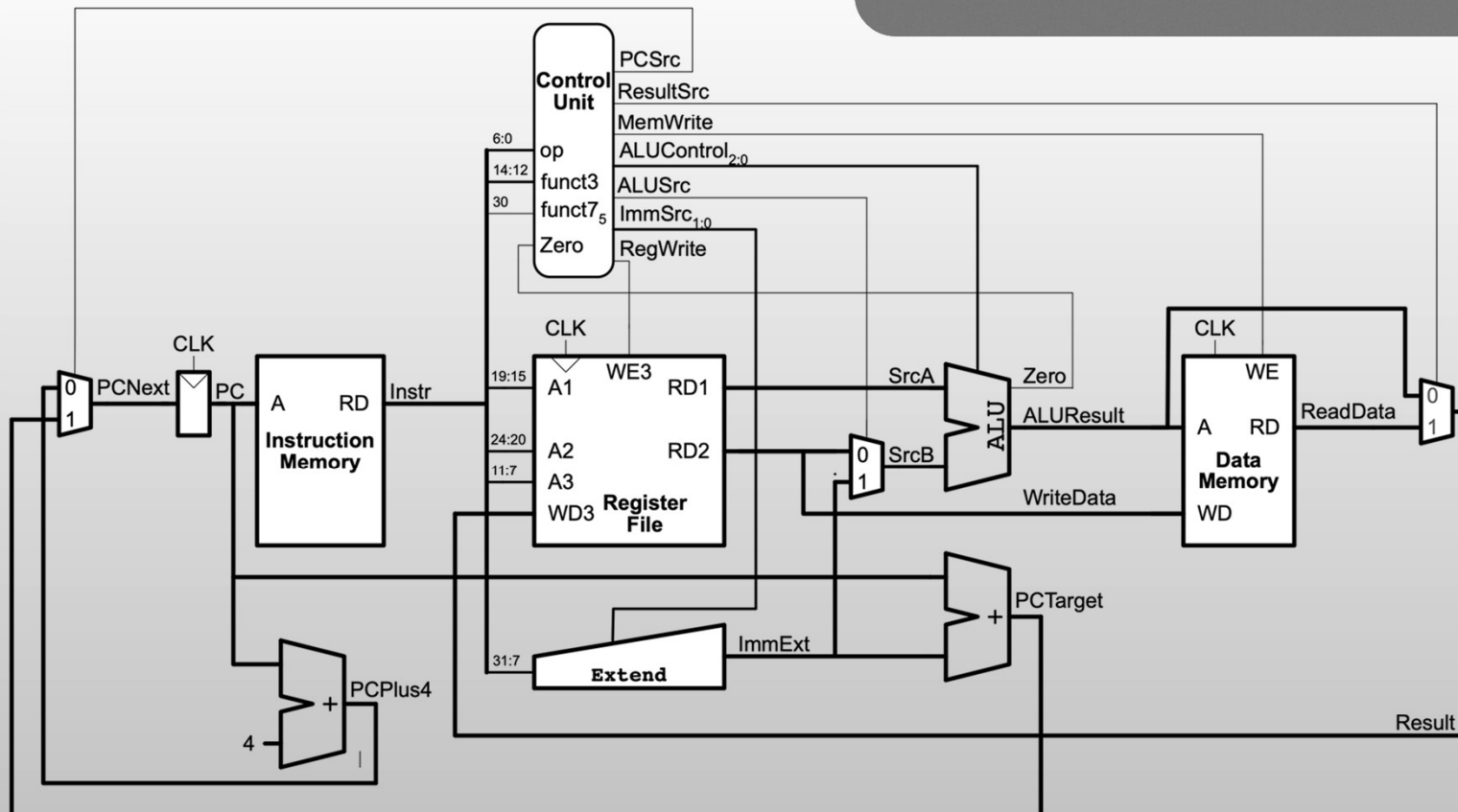
# Simple, Single-Cycle RISC

Describe behavior of all elements and any required control signals for sw t0,4(a0)


 
# Simple, Single-Cycle Processor


Describe behavior of all elements and any required control signals for write to register (a0)





 
# Simple, Single-Cycle RISC-V Computer

Consider a sequence of instructions:  
add t1,t2,t3  
lw t4, 0(sp)  
...



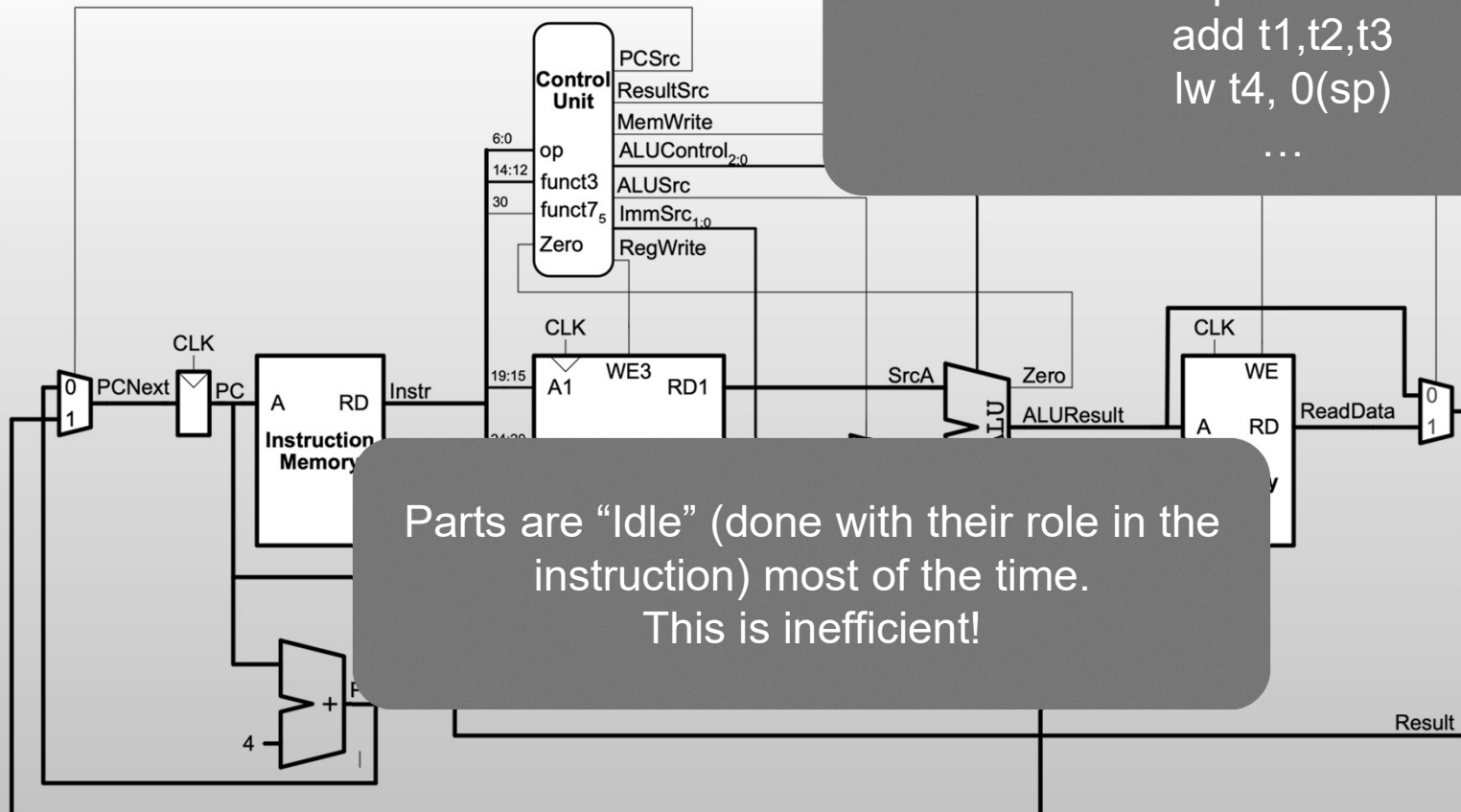
# Simple, Single-Cycle RISC-V Computer

Consider a sequence of instructions:  
add t1,t2,t3  
lw t4, 0(sp)  
...




Parts are "Idle" (done with their role in the instruction) most of the time.  
This is inefficient!


# Simple, Single-Cycle: Inefficient!

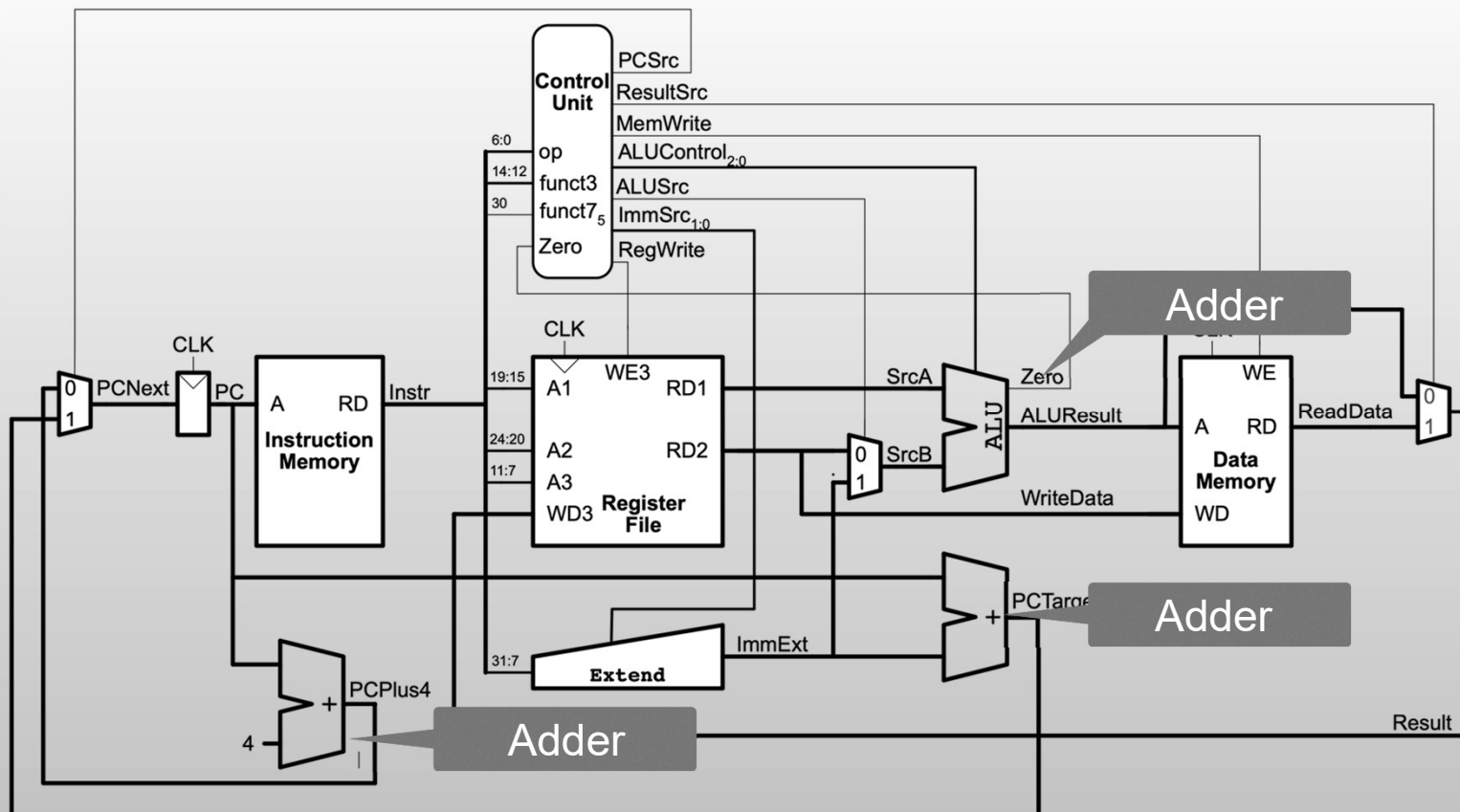


# Simple, Single-Cycle: Inefficient!

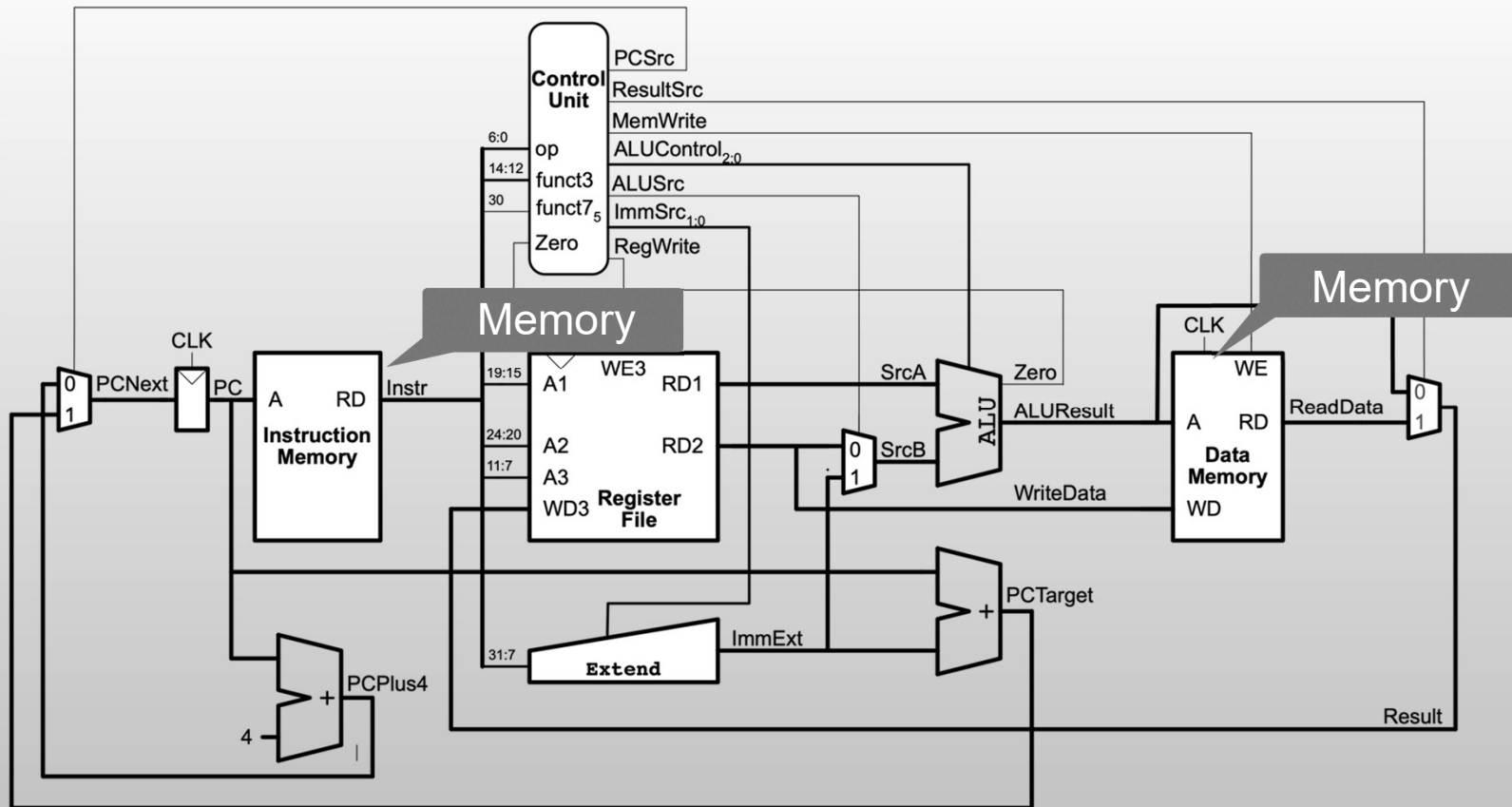


# Simple, Single-Cycle RISC-V Computer

 

# Multi-Cycle RISC-V Computer

 


# Process

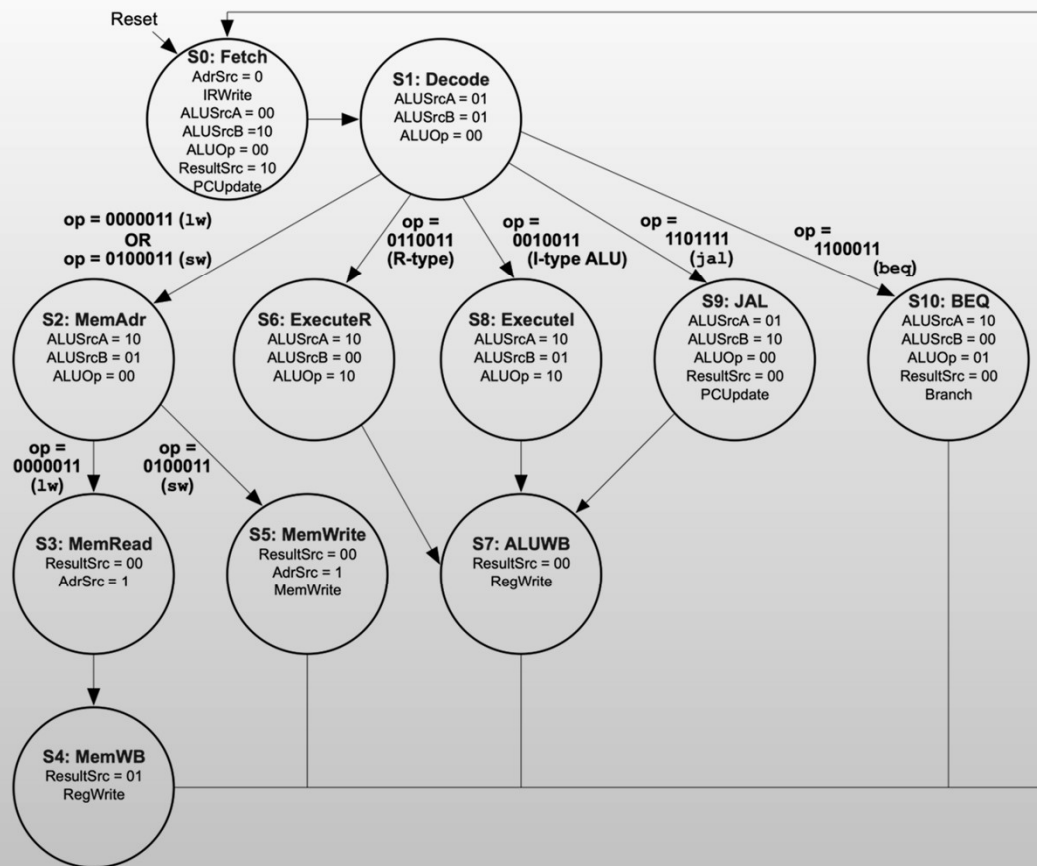


# Pros/Cons of Multi-Cycle

- Instructions take only required time: Not constrained by the slowest instruction!
- A little more complex


# Process

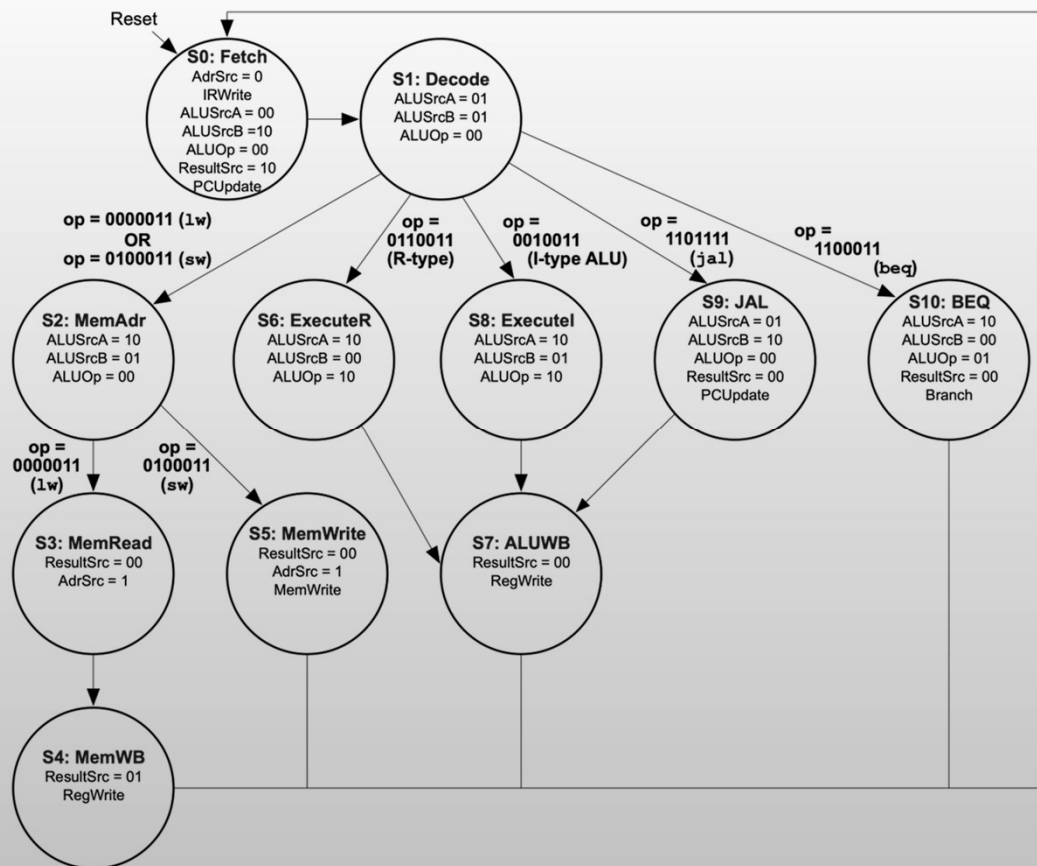



# Process: Hw 3B & 4B - Washer

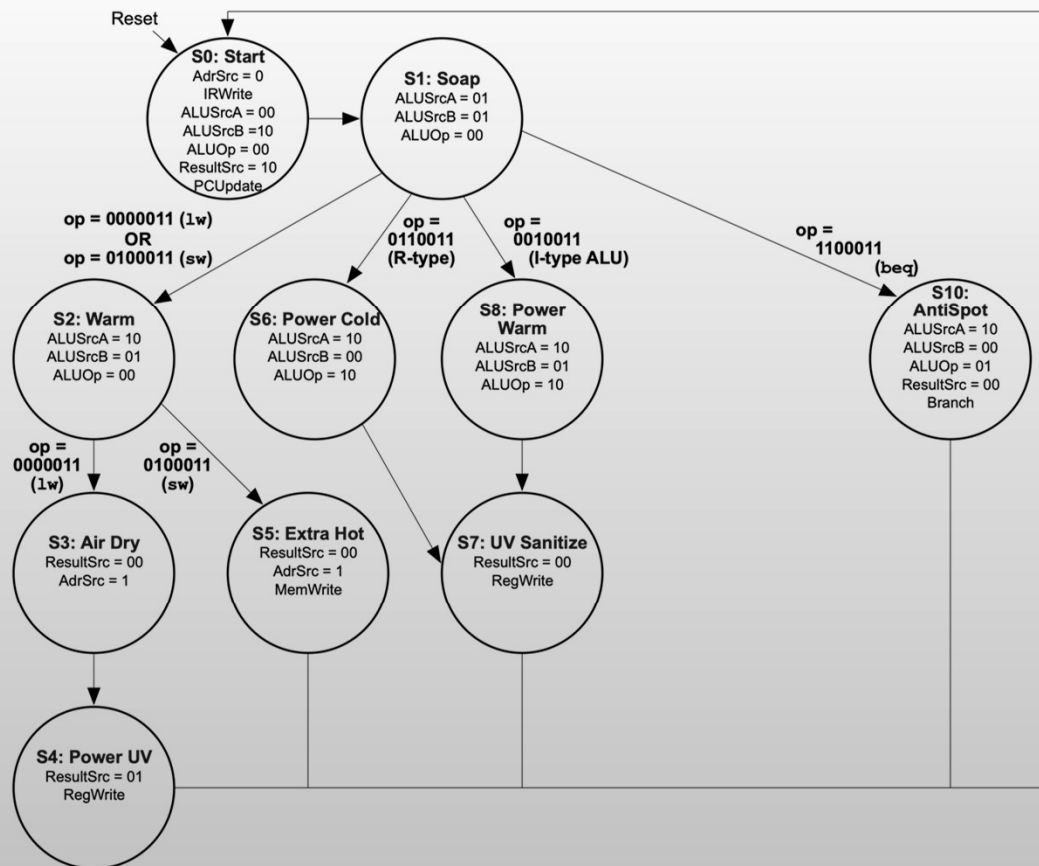

# Ex: add t0,t1,t2

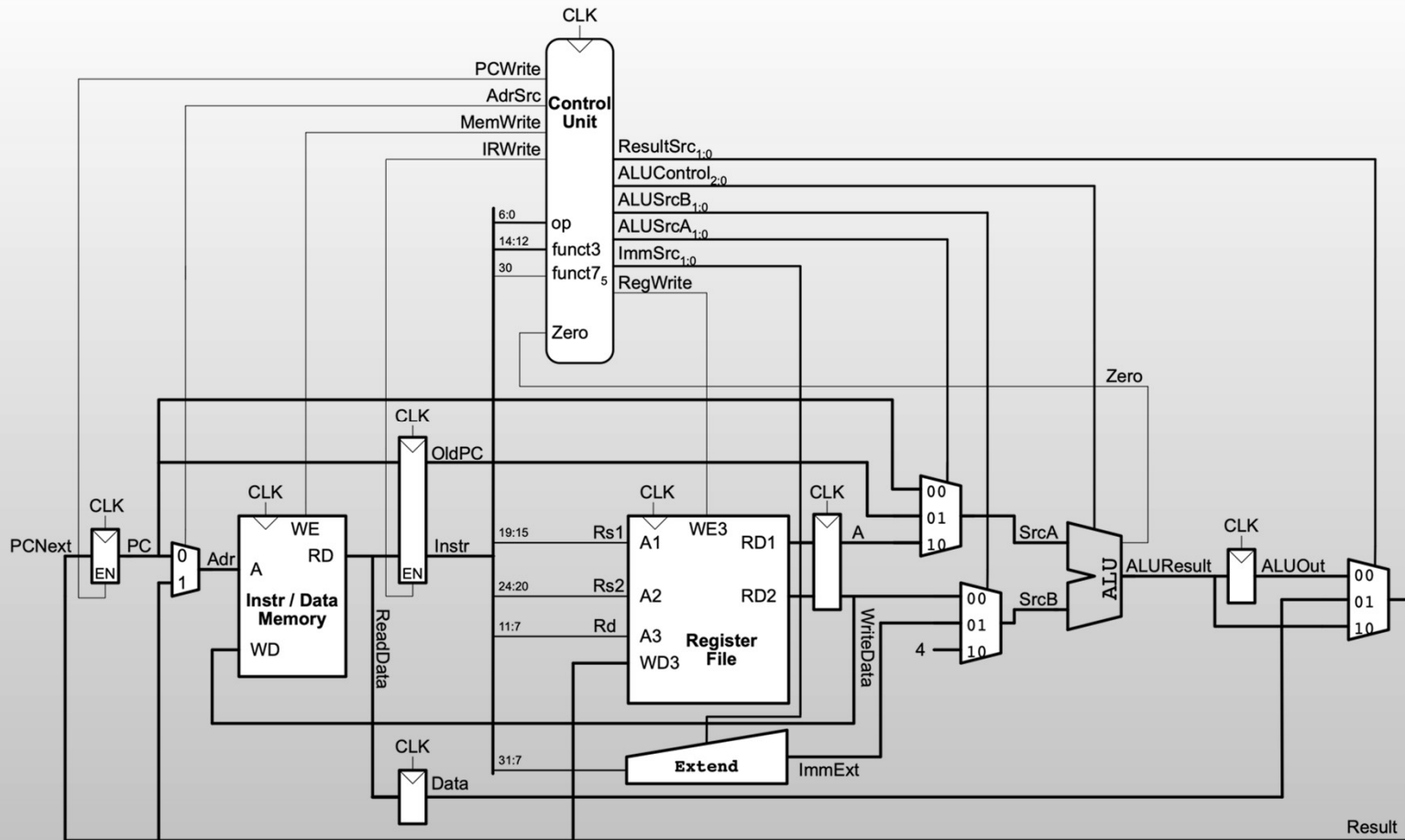


# Ex: add t0,t1,t2

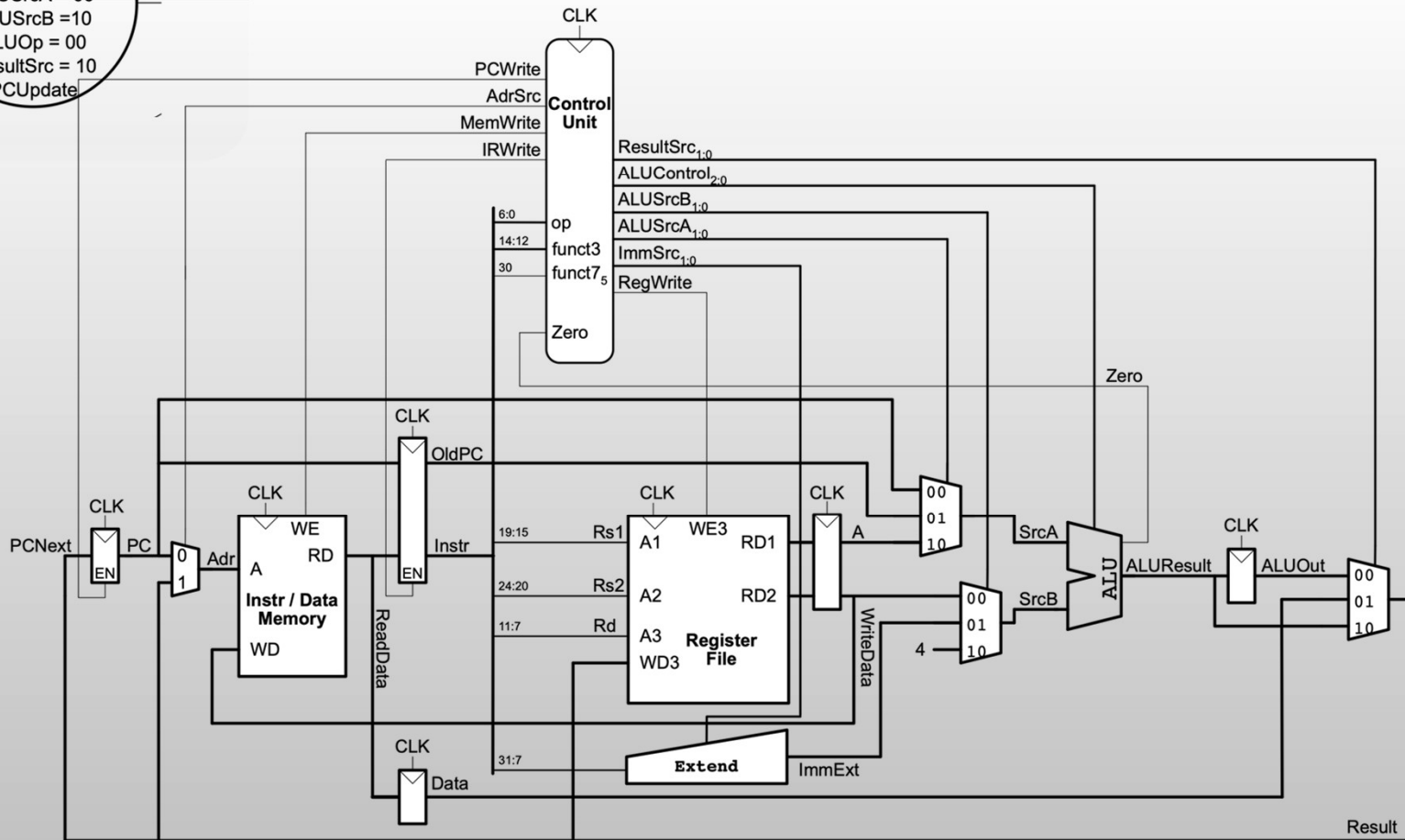 

**S1: Decode**

ALUSrcA = 01  
ALUSrcB = 01  
ALUOp = 00


# Ex: add t0,t1,t2

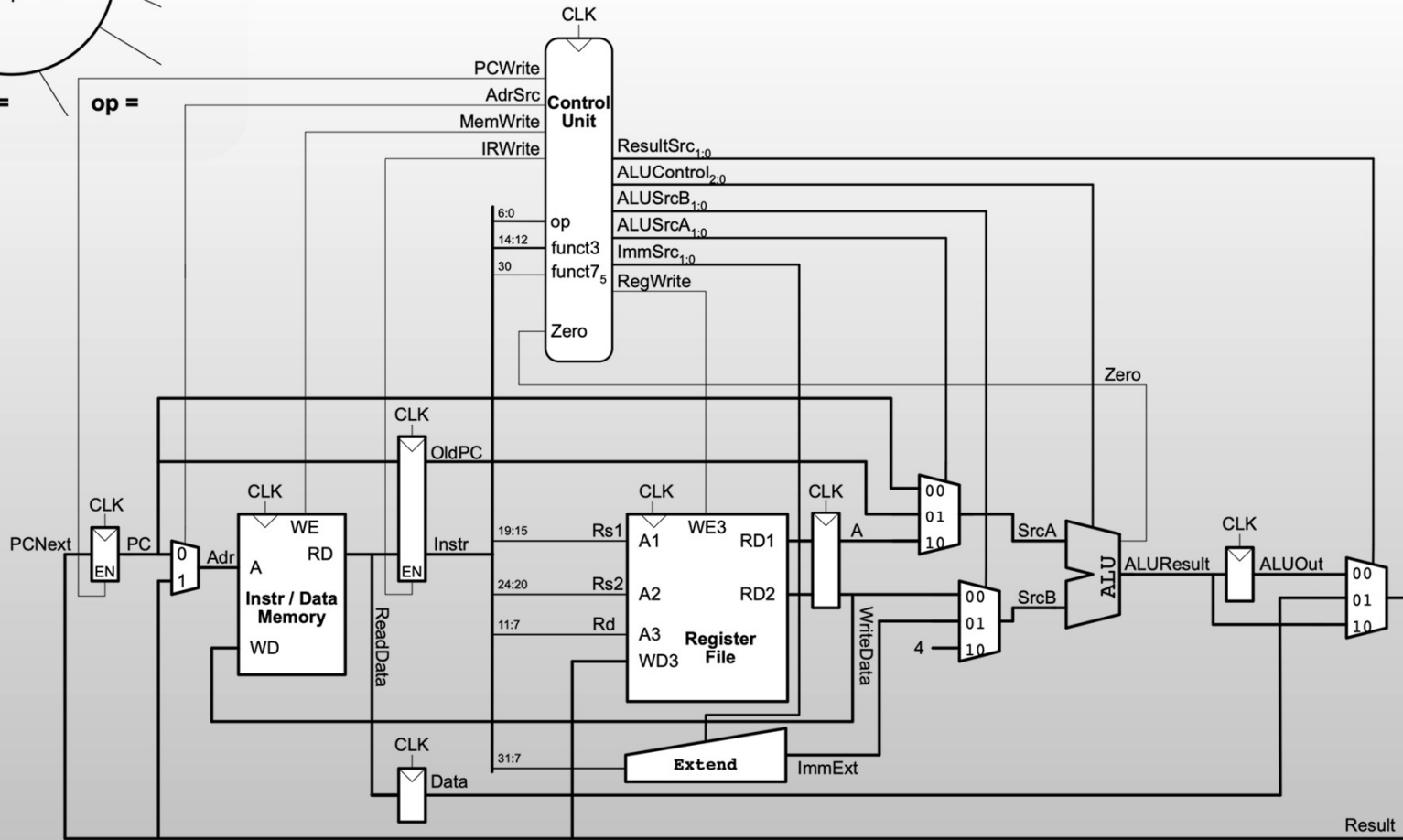

op =  
0110011  
(R-type)


S6: ExecuteR  
ALUSrcA = 10  
ALUSrcB = 00  
ALUOp = 10

# Ex: add t0,t1,t2

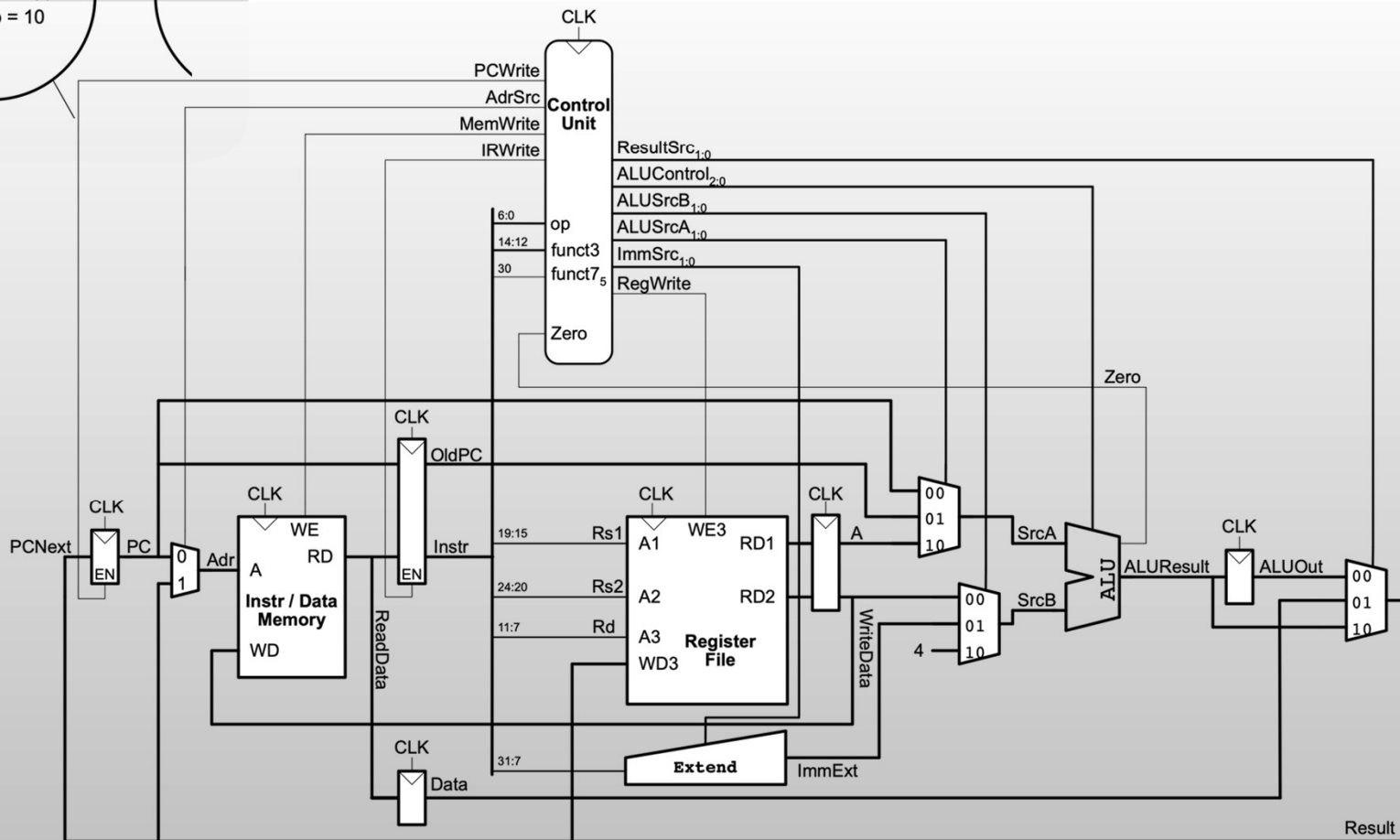

**S7: ALUWB**  
ResultSrc = 00  
RegWrite

# Ex: add t0,t1,t2

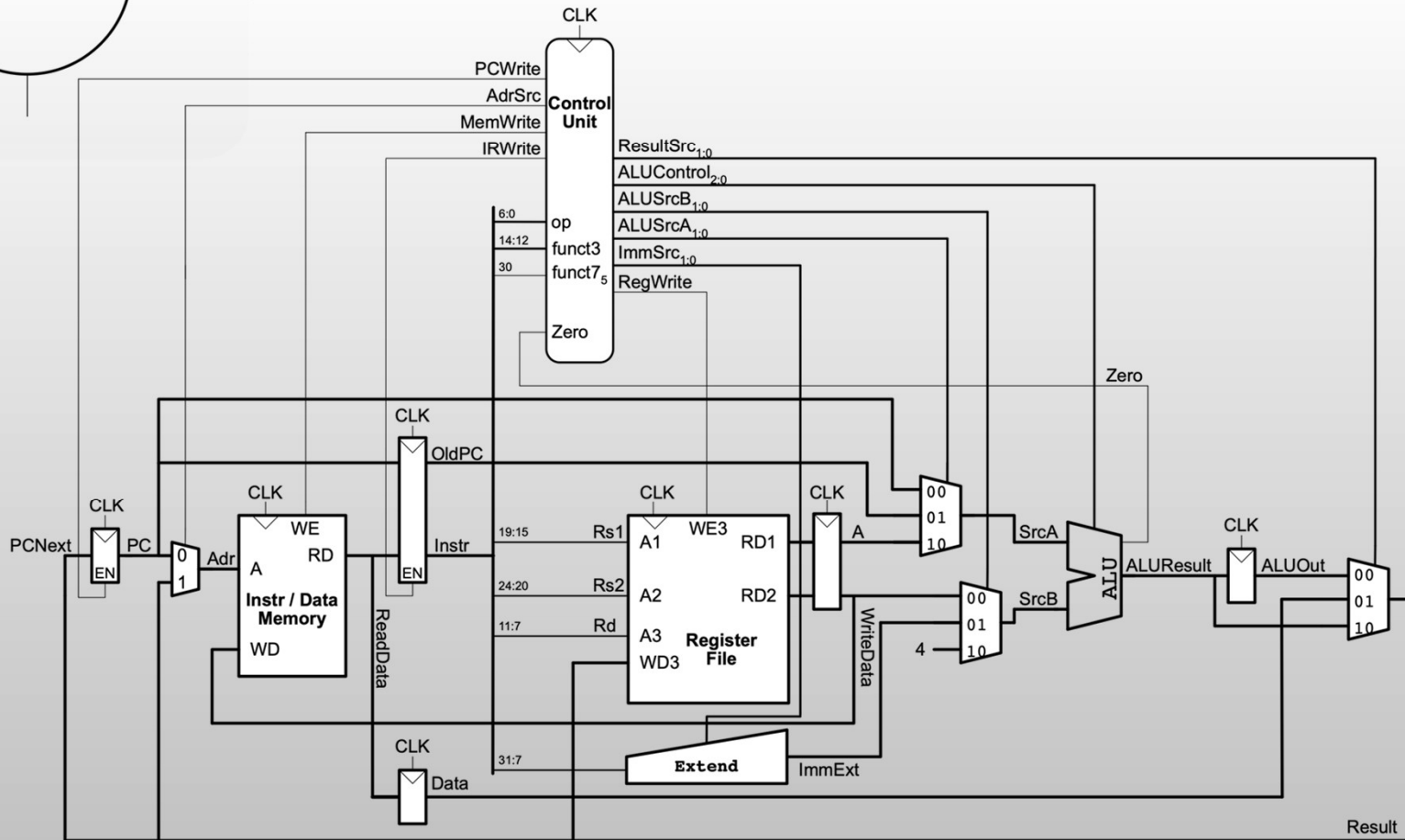

# Questions

- The register file inputs and outputs are a bit confusing to me: A1-A3, Rd1, Rd2.
- How exactly do control signals get generated from an instruction step-by-step (not just conceptually, but concretely in hardware)?
- If multicycle solves the problem of long clock cycles but incurs many CPI, which cause slower overall performance, how do we evaluate the trade-offs between multicycle and single-cycle?
- Are there still any single-cycle and multicycle architectural hardware selling now?
- How are hazards handled and how much pipelining actually improves performance in real cases?